

### **Tutorial 2:**

Q1) A 220 V, 500 A, 600 RPM separately excited motor has armature and field resistance of 0.02 and 10  $\Omega$  respectively. The load torque is given by the expression  $T_L = 2000 - 2N$ , N-m, where N is the speed in RPM. Speeds below the rated are obtained by the armature voltage control and speeds above rated are obtained by the field control.

- (i) Calculate the motor terminal voltage and armature current when speed is 450 rpm
- (ii) Calculate motor terminal voltage and current when the speed is 750 rpm.

Q2) A 2-pole separately excited dc motor has the ratings of 220 V, 100 A and 750 rpm. Resistance of the armature is 0.1  $\Omega$ . The motor has two field coils which are normally connected in parallel. It is used to drive a load whose torque is expressed as  $T_L = 5000 - 0.3N$ , N-m where N is the motor speed in rpm. Speeds below and above rated are obtained by armature voltage control and by connecting the two field windings in series respectively.

- (i) Calculate the motor armature current and speed when the armature voltage is reduced to 110 V
- (ii) Calculate the motor speed and the current when the field coils are connected in series.

3) A 220 V, 1500 rpm, 50 A separately excited motor with armature resistance of 0.5  $\Omega$ , is fed from a 3-phase fully controlled rectifier. Available ac source has a line voltage of 440 V, 50 Hz. A star delta connected transformer is used to feed the armature so that the motor terminal voltage equals rated voltage when converter firing angle is zero.

- (i) calculate the transformer turns ratio
- (ii) Determine the value of firing angle when: (a) motor is running at 1200 rpm and the rated torque (b) When motor is running at 8000 rpm and twice the rated torque.

Assume continuous conduction.