

Development of Truth Tables

Goal: Given a word problem, develop a truth table. Why? Truth table → Minterm or Maxterm list → Simplified SOP or POS function → Circuit.

Ex1. A system has 3 inputs A , B , and C , and one output Z , such that $Z = 1$ iff exactly two of the inputs are HIGH (1). Create its truth table.

Ex2. A system has 4 inputs and three outputs. The first 2 inputs (X_1 , X_0) represent a two 2-bit binary number, and the last 2 inputs (Y_1 , Y_0) represent another 2-bit number. The 3 outputs are defined as follows:

$F = 1$ iff the two numbers differ by exactly 2.

$G = 1$ iff the two numbers are equal.

$H = 1$ iff the second number is larger than the first.

Create its truth table.

2.5: From Truth Table to Algebraic Expressions

Goal: Given the truth table of a function, derive its algebraic expression.

Minterm: a canonical product term (a *product term* where every input variable appears once).

For a **2**-input function, there are 4 minterms. Ex: For the function $F(a,b)$

Minterm	Looks like	Designation
$a'b'$		
$a'b$		
$a b'$		
$a b$		

For minterms:
0 = variable is primed
1 = no prime

For a **3**-input function, there are 8 minterms. Ex: For the function $F(a,b,c)$

Minterm	Looks like	Designation
$a'b'c'$		
$a'b'c$		
$a'b c'$		
$a'b c$		
$a b'c'$		
$a b'c$		
$a b c'$		
$a b c$		

Maxterm: a canonical sum term (a *sum term* where every input variable appears once).

For a **2**-input function, there are 4 maxterms. Ex: For the function $F(a,b)$

Maxterm	Looks like	Designation
$a + b$		
$a + b'$		
$a' + b$		
$a' + b'$		

For maxterms:
0 = no prime
1 = variable is primed

For a **3**-input function, there are 8 maxterms. Ex: For the function $F(a,b,c)$

Maxterm	Looks like	Designation
$a + b + c$		
$a + b + c'$		
$a + b' + c$		
$a + b' + c'$		
$a' + b + c$		
$a' + b + c'$		
$a' + b' + c$		
$a' + b' + c'$		

- **Sum of minterms (also known as minterm list)**

Look for the 1's in the truth table.

<i>a</i>	<i>b</i>	<i>F</i>
0	0	0
0	1	1
1	0	1
1	1	1

$F(a,b) =$

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$F(A,B,C) =$

- **Product of maxterms (also known as maxterm list)**

Look for the 0's in the truth table.

<i>a</i>	<i>b</i>	<i>F</i>
0	0	0
0	1	1
1	0	1
1	1	1

$F(a,b) =$

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$F(A,B,C) =$

Summary

A function can be expressed in minterms/SOP *or* in maxterms/POS forms:

- Look for 1's in truth table → minterm list → leads to an SOP expression
- Look for 0's in truth table → maxterm list → leads to an POS expression

Once the SOP or POS expression is obtained, a logic circuit can be derived.

More Examples:

Ex 1. (see p. 62). Given $F(w,x,y,z) = \sum m(0,1,5,9,11,15)$, derive:


- 1) SOP equation 2) Maxterm list 3) POS equation

Ex 2. Given $F(x,y,z) = \pi M(0,1,4,7)$, derive:

- 1) SOP equation 3) Minterm list
2) POS equation 4) Complement function $F'(x,y,z)$ in minterm list form

 
2.6: NAND, NOR and XOR Logic Functions (Derived Functions)

NAND = NOT-AND (AND gate followed with a NOT gate)



Logic Symbol


Truth Table

 

Alternate (Equivalent) Logic Symbol


Timing Diagram

 NOR = NOT-OR (OR gate followed with a NOT gate)



Logic Symbol

Truth Table

 


Alternate (Equivalent) Logic Symbol

Timing Diagram

NAND gates and NOR gates can have more than 2 inputs.

Example: 4-input NAND

 

Truth table has 16 combinations.
 Output is 0 only for one input combination. Which one?

In practice, most circuits are implemented using only either NAND gates or NOR gates!!! [NAND is most preferred, because it is the fastest gate.]

Circuit Implementation using NAND gates only

Any two-level AND/OR circuit can be converted into a NAND-gate circuit implementation.

1. Replace all gates by NAND gates
2. Any input going directly into original OR gates are complemented.

Ex: $F(x,y,z) = x'y + xy' + z$ [SOP form \Rightarrow Two-level AND/OR circuit]

Circuit Implementation using NOR gates only

Any two-level OR/AND circuit can be converted into a NAND-gate circuit implementation.


1. Replace all gates by NOR gates
2. Any input going directly into original AND gates is complemented.

Ex: $G(x,y,z) = (x + y')(y' + z)(x')$ [POS form \Rightarrow Two-level OR/AND circuit]

Multi-level circuits are trickier to implement using single-type gate.

Ex: $F(w,x,y,z) = wx(y+z) + x'y$ [Neither SOP nor POS form]

 XOR = Exclusive OR (can have 2 or more inputs)



Logic Symbol

Truth Table

Timing Diagram

Definition of XOR function: $a \oplus b = a b' + a' b = \Sigma m(1,2) = \prod M(\quad)$

XOR function is both commutative and associative.

$$a \oplus b = b \oplus a$$

$$a \oplus b \oplus c = (a \oplus b) \oplus c = a \oplus (b \oplus c)$$

Useful properties:

$$(a \oplus b)' =$$

$$a' \oplus b =$$

$$a \oplus b' =$$

$$a \oplus 1 =$$

$$a \oplus 0 =$$

Example using XOR: $G(x,y,z) = (x \oplus y')(z')$

What is the minterm list?