

Tutorial 2:

Q1) A 220 V, 500 A, 600 RPM separately excited motor has armature and field resistance of 0.02 and 10 Ω respectively. The load torque is given by the expression $T_L = 2000 - 2N$, N-m, where N is the speed in RPM. Speeds below the rated are obtained by the armature voltage control and speeds above rated are obtained by the field control.

- (i) Calculate the motor terminal voltage and armature current when speed is 450 rpm
- (ii) Calculate motor terminal voltage and current when the speed is 750 rpm.

Q2) A 2-pole separately excited dc motor has the ratings of 220 V, 100 A and 750 rpm. Resistance of the armature is 0.1 Ω . The motor has two field coils which are normally connected in parallel. It is used to drive a load whose torque is expressed as $T_L = 5000 - 0.3N$, N-m where N is the motor speed in rpm. Speeds below and above rated are obtained by armature voltage control and by connecting the two field windings in series respectively.

- (i) Calculate the motor armature current and speed when the armature voltage is reduced to 110 V
- (ii) Calculate the motor speed and the current when the field coils are connected in series.

3) A 220 V, 1500 rpm, 50 A separately excited motor with armature resistance of 0.5 Ω , is fed from a 3-phase fully controlled rectifier. Available ac source has a line voltage of 440 V, 50 Hz. A star delta connected transformer is used to feed the armature so that the motor terminal voltage equals rated voltage when converter firing angle is zero.

- (i) calculate the transformer turns ratio
- (ii) Determine the value of firing angle when: (a) motor is running at 1200 rpm and the rated torque (b) When motor is running at 8000 rpm and twice the rated torque.

Assume continuous conduction.

SOLUTIONS:

1)

Solution

(i) At 450 rpm, $T_L = 2000 - 2 \times 450 = 1100$ N-m

At rated operation $E_1 = 220 - 500 \times 0.02 = 210$ V

$$\text{Rated torque} = \frac{E_1 I_{a1}}{\omega_{m1}} = \frac{210 \times 500}{600 \times 2\pi/60} = 1671 \text{ N-m}$$

For a torque of 1100 N-m, $I_{a2} = \frac{1100}{1671} \times 500 = 329$ A

At 450 rpm, $E_2 = \frac{450}{600} \times 210 = 157.5$

$$V = E_2 + I_{a2} R_a = 157.5 + 329 \times 0.02 = 164 \text{ V}$$

(ii) At 750 rpm $T_L = 2000 - 2 \times 750 = 500$ N-m

At this operating point, let the flux and armature current be ϕ' and I'_a respectively. Then

$$K_e \phi' I'_a = 500 \quad (i)$$

From rated operation

$$K_e \phi_1 = \frac{210}{600 \times 2\pi/60} = 3.342$$

Further at 750 rpm, $\omega'_m = \frac{750}{60} \times 2\pi = 78.54$ and $V = K_e \phi' \omega'_m + I'_a R_a$

$$\text{or} \quad 220 = 78.54 K_e \phi' + 0.02 I'_a$$

Substituting from Eq. (i)

$$220 = 78.54 \times \frac{500}{I'_a} + 0.02 I'_a$$

$$\text{or} \quad 0.02 I'^2_a - 220 I'_a + 39270 = 0$$

This equation has solutions 181.5 A and 21647 A. Ignoring the unfeasible value gives

$$I'_a = 181.5$$

$$\text{From Eq. (i)} \quad K_e \phi' = \frac{500}{181.5} = 2.755$$

$$\text{Field voltage} = 220 \times \frac{K_e \phi'}{K_e \phi_1} = 220 \times \frac{2.755}{3.342} = 181.3 \text{ V}$$

2)

Solution

At rated operation, $E_1 = 220 - 100 \times 0.1 = 210 \text{ V}$

$$\omega_{m1} = \frac{750}{60} \times 2\pi = 25\pi$$

$$K_e \phi_1 = K = \frac{E_1}{\omega_{m1}} = \frac{210}{25\pi} = 2.674$$

(i) Let the motor speed and current be N_2 and I_{a2} , respectively.

$$E_2 = K\omega_{m2} = 2.674 \times \frac{N_2 \times 2\pi}{60} = 0.28N_2$$

$$V = E_2 + I_{a2}R_a$$

or

$$110 = 0.28N_2 + 0.1I_{a2} \quad (1)$$

Since

$$T = T_L$$

$$KI_a = 500 - 0.3N$$

or

$$2.674I_{a2} = 500 - 0.3N_2$$

or

$$500 = 0.3N_2 + 2.674I_{a2} \quad (2)$$

Simultaneous solution of Eq. (1) and (2) gives

$$I_{a2} = 148.9 \text{ A} \quad \text{and} \quad N_2 = 339.7 \text{ rpm}$$

(ii) When field coils are connected in series

$$K = \frac{2.674}{2} = 1.337$$

If armature current and speeds are I_{a3} and N_3

$$E_3 = 1.337 N_3 \times \frac{2\pi}{60} = 0.14N_3$$

$$V = E_3 + I_{a3}R'_a$$

or

$$220 = 0.14N_3 + 0.1I_{a3} \quad (3)$$

Since

$$T = T_L$$

$$1.337I_{a3} = 500 - 0.3N_3$$

or

$$500 = 0.3N_3 + 1.337I_{a3} \quad (4)$$

Simultaneous solution of Eqs. (3) and (4) yields

$$I_{a3} = 25.48 \text{ A} \quad \text{and} \quad N = 1553.2 \text{ rpm}$$

3)

Solution

For 3-phase fully-controlled rectifier from Eq. (5.97)

$$V_m = \frac{\pi}{3} \cdot \frac{V_a}{\cos \alpha}$$

For rated motor terminal voltage $\alpha = 0^\circ$

$$V_m = \frac{\pi}{3} \frac{220}{\cos 0^\circ} = 230.4 \text{ V}$$

rms converter input voltage between lines = $230.4/\sqrt{2} = 162.9 \text{ V}$

For star-delta transformer connection, ratio of turns between phase windings of primary and secondary = $\frac{440/\sqrt{3}}{162.9} = 1.559$.

(ii) (a) At 1500 rpm

$$E = 220 - 0.5 \times 50 = 195 \text{ V}$$

At 1200 rpm

$$E = \frac{1200}{1500} \times 195 = 156 \text{ V}$$

$$V_a = E + I_a R_a = 156 + 50 \times 0.5 = 181 \text{ V}$$

Since

$$V_a = \frac{3}{\pi} V_m \cos \alpha$$

$$\cos \alpha = \frac{\pi}{3} \cdot \frac{V_a}{V_m} = \frac{\pi}{3} \times \frac{181}{230.4} = 0.8227$$

or

$$\alpha = 34.65^\circ$$

(b) At - 800 rpm

$$E = \frac{-800}{1500} \times 195 = -104 \text{ V}$$

$$V_a = E + I_a R_a = -104 + 100 \times 0.5 = -54 \text{ V}$$

From Eq. (i)

$$\cos \alpha = \frac{\pi}{3} \cdot \frac{V_a}{V_m} = \frac{\pi}{3} \times \frac{-54}{230.4} = -0.2454$$

or

$$\alpha = 104.20^\circ$$