


CircuitMaker 6 Student Version – Basic Digital Logic Tutorial EE244, Digital Logic Design Prof. Kam F. Yee, Montgomery College

CircuitMaker is a schematic capture and circuit simulation computer tool. The free Student Version has a limitation of 50 devices per circuit.

This basic tutorial will provide very basic guidance for installation of the software, and creation and simulation of a basic digital circuit.

1. Install CircuitMaker (a circuit design tool)
2. Create a circuit for $F(a,b) = a b' + a'b$
3. Test the circuit (circuit simulation)

<i>a</i>	<i>b</i>	<i>F</i>
0	0	0
0	1	1
1	0	1
1	1	0

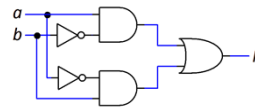


03/06/2014

1

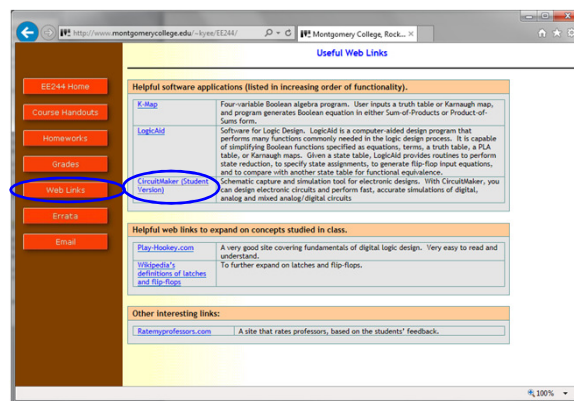1. Installing CircuitMaker

Install the software from the EE244 Course Website:

<http://www.montgomerycollege.edu/~kyee/EE244>




03/06/2014

2

2. Creating a Simple Logic Circuit

Start the CircuitMaker software.

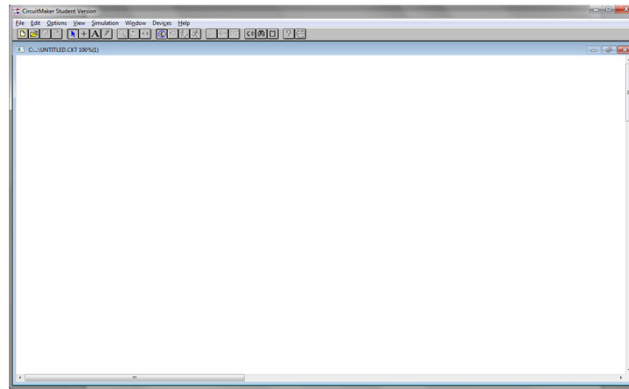


03/06/2014

3

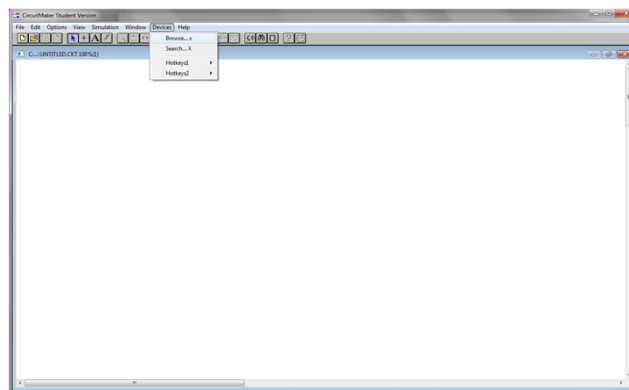2. Creating a Simple Logic Circuit (Continued)

Add components: Select **Devices** → **Browse** from top menu bar (or use shortcut lowercase x).




03/06/2014

4

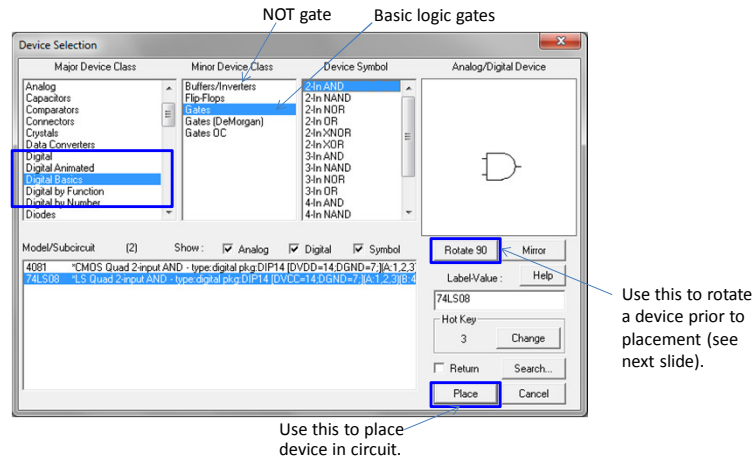2. Creating a Simple Logic Circuit (Continued)

Most digital devices can be found in the 'Digital' libraries.




03/06/2014

5

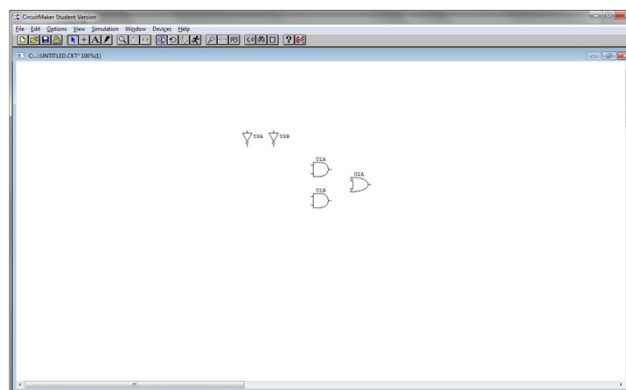2. Creating a Simple Logic Circuit (Continued)

Add 2-input AND gates, 2-input OR gate, and NOT gates.





03/06/2014

6

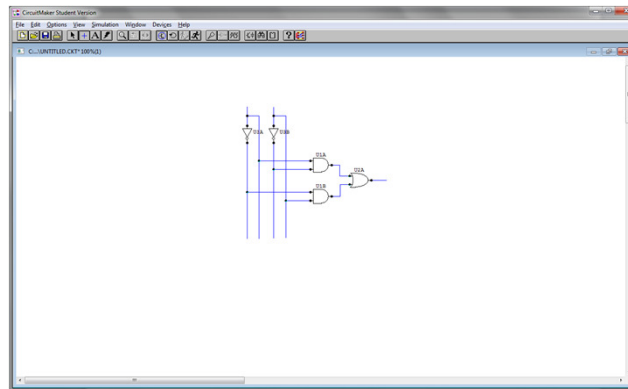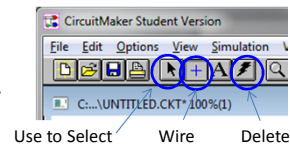2. Creating a Simple Logic Circuit (Continued)

Make wiring connections using the **Wire** tool.
Aesthetics is important (takes some practice).




03/06/2014

7

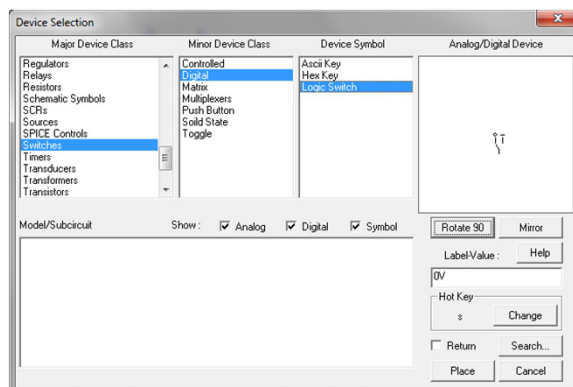2. Creating a Simple Logic Circuit (Continued)

Add input switches. Rotate them as shown.




03/06/2014

8

2. Creating a Simple Logic Circuit (Continued)

Place rotated switches in the circuit.

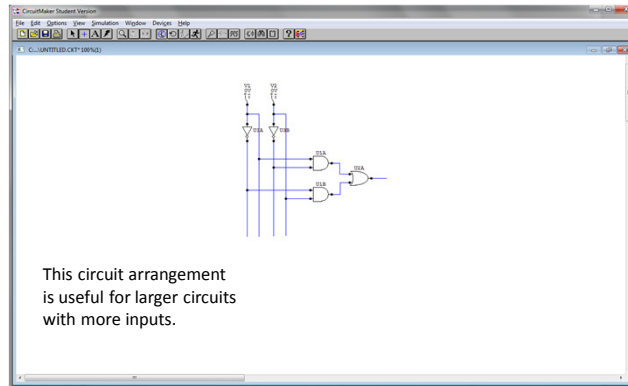


03/06/2014

9

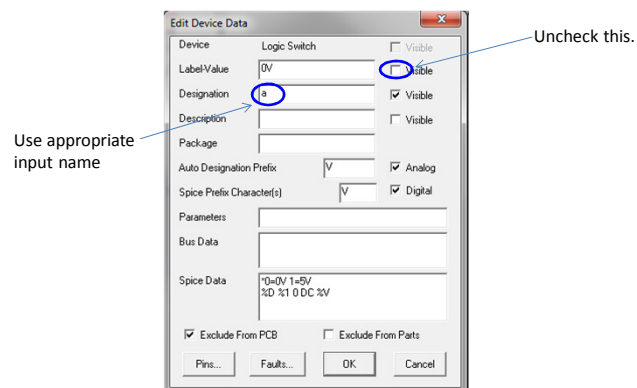2. Creating a Simple Logic Circuit (Continued)

Double click on switch to change properties. Do this for both switches.




03/06/2014

10

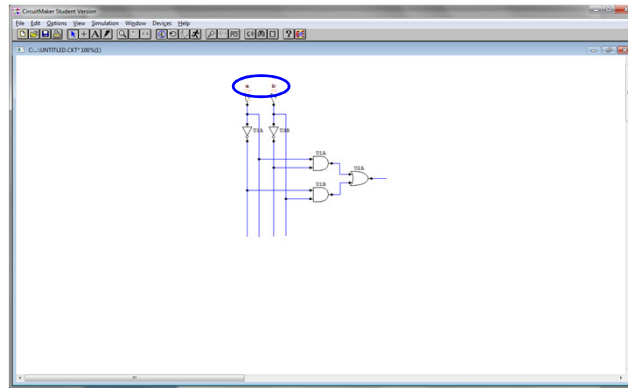2. Creating a Simple Logic Circuit (Continued)

Inputs have appropriate names that match desired design.




03/06/2014

11

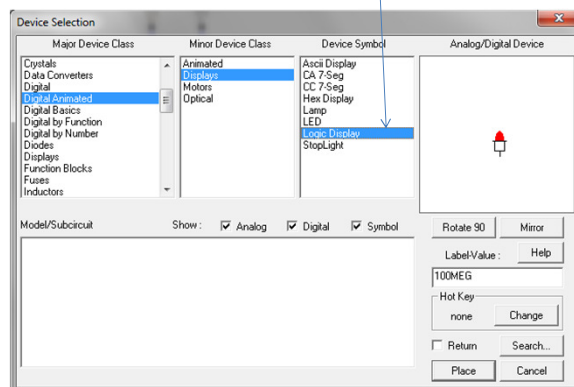2. Creating a Simple Logic Circuit (Continued)

Add LED for the output. Use the **Logic Display** device.




03/06/2014

12

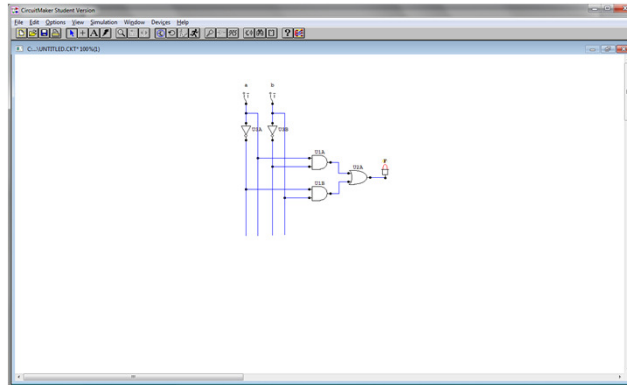2. Creating a Simple Logic Circuit (Continued)

Place the LED and connect it to the output of the circuit. Right click on the LED, and select “**Edit Device Data**” to change its default name (“L1”) to the desired name (“F”).



03/06/2014


13

2. Creating a Simple Logic Circuit (Continued)

Circuit is complete at this point. There are two optional things that can be done to get a “cleaner” look (this is for aesthetics only):

- Uncheck the **Show Pin Dots** (shortcut: F5 key) to remove unneeded dots.
- Right click on every device, select **Edit Device Data**, and uncheck **Designation** so that those U1A, U1B, U2A, etc, names are not visible.

Don't show
pin dots for a
cleaner look

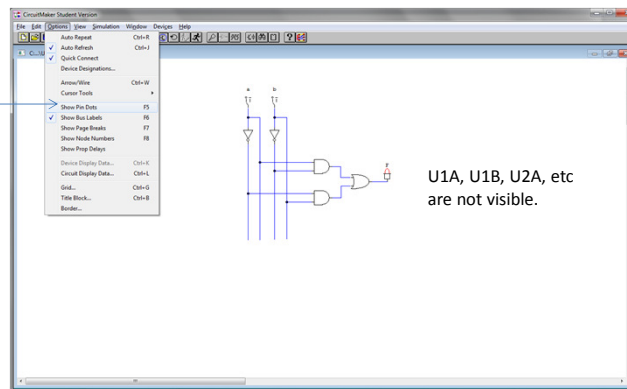

U1A, U1B, U2A, etc
are not visible.


03/06/2014

14

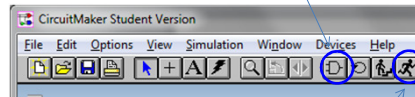3. Test the Circuit

Important: Must set to Digital mode in order to simulate digital circuits.

Click to show an AND gate
(AND = digital mode)




Click on Run/Stop to start circuit simulation.
Click again to end circuit simulation.
To edit the circuit (make additional changes),
simulation must be stopped.

03/06/2014

15

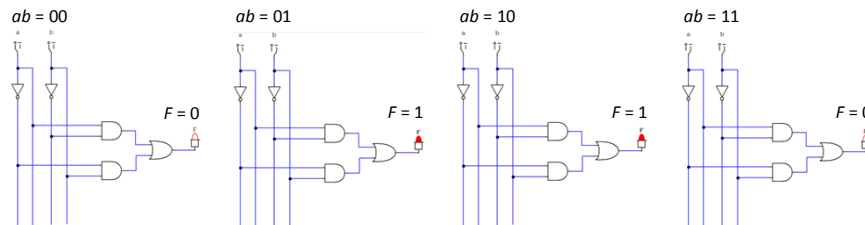3. Test the Circuit (Continued)

For circuits with few inputs/outputs (as is in this example), one can simply flip switches and observe the output, for every input combination. For more complex cases, a timing diagram might be more appropriate (not covered in this tutorial).



a	b	F
0	0	0
0	1	1
1	0	1
1	1	0

Matches the desired design.


03/06/2014

16

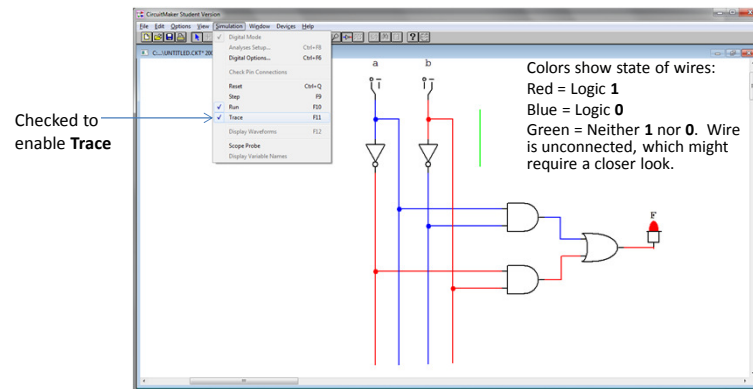3. Test the Circuit (Continued)

More than likely, a circuit will not work correctly the first time. You must troubleshoot the circuit in this case.

During simulation, use the **Trace** tool to see state of each wire.



03/06/2014

17